
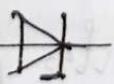


Schottky Diode & Zener Diode (Vid - 31):-

- * Schottky Diode \rightarrow  IN5819
 - * very small conduction loss, low forward voltage drop
 - * Extremely fast switching
 - * High frequency operation
 - * Boost converter - boost a low DC voltage to higher DC voltage - coil, MOSFET, Diode, Capacitor
 - * ~~Low~~ Low blocking voltage \rightarrow cons

- * Zener Diode : 
 - * Zener Voltage

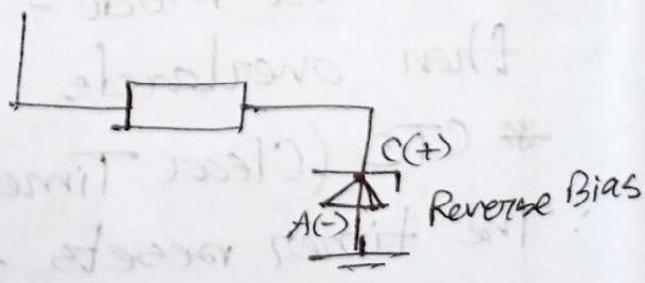

④ Relays and Optocouplers (Vid - 32)

Relay - electromechanical switch

- * sits next to 4 pin ICs

* A coil, two contacts

- * NC - Normally Closed, NO - Normally Open

* contacts open-close via magnetic field

* add flyback diode parallel to coil

- * MOSFET and triac causes power loss

* Galvanically isolated

Optocoupler:

- * Inside \rightarrow led, photosensitive sensor \rightarrow triac / transistor

* Input - output galvanically isolated

* switch faster than relays

* need less activation current

⑤ Strain Gauge / Load Cell and how to use them to measure weight:- (Vid - 33)

* Resistance $120\ \Omega / 370\ \Omega / 1000\ \Omega$

* Resistance changes as the shape changes

* $F \propto E \propto R$ because

* Wheatstone Bridge

* Temperature sensitive but rapid

* Half Bridge

Load Cell :- * aluminium profile

* Wheatstone Bridge is attached

* Connect with HX711 break board - amplifier
ADC circuit

④ Two-position Controller and PID Controller (Vid - 34) :-

* PID - Proportional Integral Derivative

* $F_{mg} = F_a$, gets closer to magnet + turns off
gets far - turns on

* P controller \Rightarrow Output = (Set P - Act v). K_p

* I controller \Rightarrow Diminishes gap with set point

* D controller \Rightarrow Works with the change

⑤ Schmitt Trigger and When to use (Vid - 35)

* comparator resistor \rightarrow Schmitt Trigger

* two threshold values

* avoid noise caused oscillation

* Mechanical switch creates noise oscillation,
Schmitt trigger helps in smooth transition

Q) SPI and How to Use it (Vid-36)

- * SPI \Rightarrow Serial Peripheral Interface
- * 4 main lines:- - MOSI, MISO, SCLK, SS/CS
- * full duplex communication
- * can communicate with multiple slaves
- * high speed communication simple hardware interface no need of device addressing.
- * More pins required, short distance communication and no built-in error checking

Q) What is Impedance (AC Resistance) [Vid-37]

- * Impedance - resistor in AC circuits
- * Two concepts - $\frac{\text{resistance}}{\text{real part}}$ and $\frac{\text{reactance}}{\text{imaginary}}$
- * $Z = R + jX$
- * Inductive Reactance \uparrow frequency \uparrow
- * Capacitive Reactance \downarrow frequency \uparrow
- * Impedance Triangle (Resistance, Reactance, Impedance Magnitude)
- * Capacitors cause current to lead voltage.
Inductors cause current to lag voltage

④ True, Active, Apparent & Deformed Power (Vid-3)

* Energy Multimeter - B probes, can measure electric power and also energy over time in AC appliances


* True Power / Active Power (P) :- This is the actual power consumed by resistive components in a circuit to perform work, (watts)

* Reactive Power (Q) :- Power that oscillates between the source and reactive components (inductors and capacitors), doesn't perform any real work, but essential for maintaining voltage level.

* Apparent Power :- (S) :- $S = \sqrt{P^2 + Q^2}$ (volt-amp)
Represents the total power supplied to the circuit

* Deformed / Distortion Power :- (D) Arises due to non-linear loads that distort the waveform of the current, e.g. electronic devices with rectifiers

* Power Triangle:

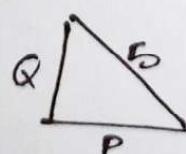

How Shift Registers Work:- (Vid-39)

* controlling large number of ~~leds~~ LEDs using shift register.

* A shift register is a digital memory circuit that takes in data serially (one bit at a time) and outputs in parallel.


* 74HC595 → 8 output pin, serial input clock input, latch input, output enable

* Multiplexing:- only one row is active at a time, shift register outputs define the lit LEDs.

* Program rapidly traverses through all rows


* NPN transistor also used

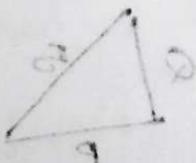* flip-flop:- NOT \rightarrow 1, NAND \rightarrow 4



RFID and NFC :- (Vid-40)


RFID → Radio Frequency Identification

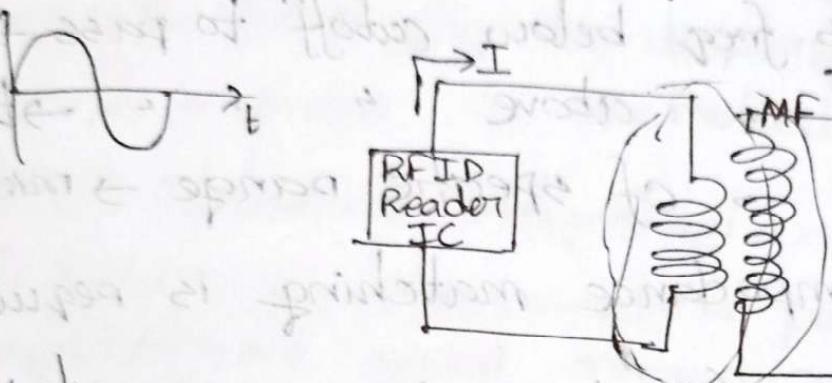

- * the tag also contains a ~~trans~~ coil or antenna and a chip
- * wireless energy transfer

* change in amplitude due to short circuit

NFC → Near Field Communication

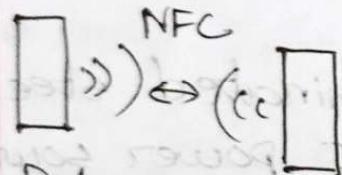

* encrypted via key

* close proximity

Dist. is mandatory

* Transaction limit

DIY Audio Crossover (Vid-41) :- (Passive Filters)

* Audio crossover - electronic circuit that divides an audio signal into separate frequency bands by directing each band to appropriate speaker drivers.

Tweeters - high freq, Midrange Driver - mid freq
Woofers - Low freq

* clearer and more accurate sound production

* Passive crossover utilize resistor, capacitor and inductors to filter audio signal.

LPF :- Allows freq below cutoff to pass \rightarrow woofer

HPF :- \rightarrow above \rightarrow tweeter

BPF :- \rightarrow of specific range \rightarrow midrange driver

* Accurate impedance matching is required


□ Transformers (Vid - 42) :-

* Transformer - steps voltage up or down through electromagnetic induction

* Parts :- core - made from laminated steel plates

Primary Coil - Connected to AC power source

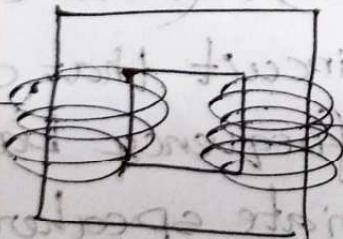Secondary Coil - Delivers transformed voltage to output load



AC flows through h coil - MF in core - changing field induces voltage in the second coil - Faraday's Second Law - Ratio of coil decides

$$\frac{V_s}{V_p} = \frac{n_s}{n_p}$$

Power loss - Copper Wire

Cores - Hysteresis Loss, Eddy Current Loss, Leakage Loss, Dielectric Loss

Controlling Mechanical 7-segment displays:- (Vid - 4B)

- * Mechanical 7-segment display - use physical segments that flip to display digits.
- * each segment is controlled by electromagnet

UART (Universal Asynchronous Receiver/Transmitter)

A hardware communication protocol that enables asynchronous serial communication

RS-485

- An electrical standard that supports serial communication over longer distance

* only defines electronic properties

A

B

Non-inverted and inverted data signal

Improving Electric Longboard with CAN bus:-


* CAN - Controller Area Network (Vid - 4C)

Features:- i) Multi-master capability - allows multiple micro controller communicate without host

ii) Error-detection.

iii) Efficient Communication

* CANH and CANL

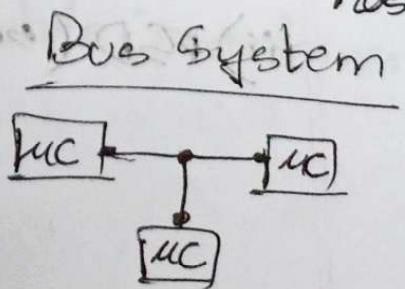

(+) - bus hardware cheap

- * No collision error, ID based system
- * Half-duplex, asynchronous communication

■ Building a Digital Music Player with I²S

(Vid - 45)

* I²S (Inter IC sound) - communication protocol designed for digital audio data transmission between ICs.


* Digital Music Player:-

- i) ESP32 Microcontroller :- main controller
- ii) MAX98357 A.I²S DAC Module :- Converts digital audio data to analog signals
- iii) Speaker - audio output

■ ESP32 - Audio I²S Library

* 3 primary lines:-

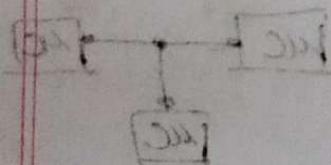
- i) SCK (Serial Clock) :- Sync data transmission
- ii) WS (Word Serial) :- Channel for stereo audio
- iii) RSD (serial data) :- Carries audio data



LNA SWS HNA

④ Asynchronous Motor / Induction Motors - (Vid - 46)

- * most widely used in the world

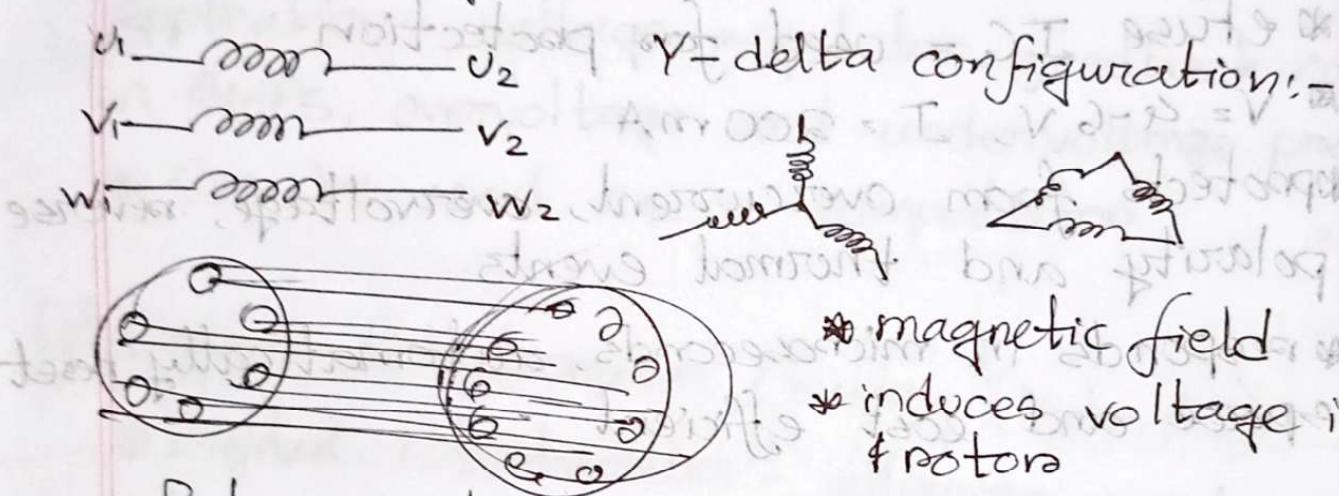

- * magnetic field induces voltage in the rotors

- * Rotor must turn slower than the stator freq.

⑤ Building a Tube Amp? (Vid - 47)

Components:- Vacuum tube (EL34/GVG)

Tube socket, Power Transformer, Output Transformer, Capacitor, Resistor, Potentiometer, Audio Input Jack, Speaker output Terminal, Chassis

- * warm and rich sound

- * produces more even-order harmonic distortion, which is pleasing to hear

- * a softer clipping behaviour while overdriven

④ eFuse + (Vid-43)

- * Using power bank to power circuit
- * eFuse IC - used for protection
- * $V = 4-6 \text{ V}$, $I = 200 \text{ mA}$
- * protects from overcurrent, overvoltage, reverse polarity and thermal events
- * responds in microseconds, automatically reset

⑤ Oscilloscope (Vid-40)

- * Visualizes voltage and current
- * Amount of channels - 04, bandwidth - 50MHz
- * low-pass filter, * sampling rate - Higher rate
- * $10 \text{ V} \rightarrow 10 \times \rightarrow 1 \text{ V}$. * scaling factors
- * cursor function - Rise Time

⑥ TL-431 (Vid-50)

A three terminal adjustable precision shunt regulator.

- * Acts like a programmable Zener diode
- * Voltage reference + Error Amplifier + Shunt Regulation

- * Maintains consistent output voltage at changing input voltage / load.
- * Application:- voltage regulator, feedback control in SMPS, overvoltage and undervoltage protection
- * Can be used as a comparator

Digital Potentiometer

- * Digital Potentiometer Guide:- (Vid - 51)
- * Digital Potentiometer - allowing resistance adjustment through digital signals
- * Used for volume control, LCD brightness adjust, turning circuits programmatically
- * I²C or SPI protocol
- * 8 pin IC, Resistor ladder network, MOSFET, Digital Interface
- * Replaces ~~manual~~ manual knob to digital commands

↳ ~~analog~~ digital input output
 12 bits → 4096 steps
 10 bits → 1024 steps
 8 bits → 256 steps
 7 bits → 128 steps
 6 bits → 64 steps
 5 bits → 32 steps
 4 bits → 16 steps
 3 bits → 8 steps
 2 bits → 4 steps
 1 bit → 2 steps

Q) Negative Voltages:- (Vid - 52)

- * Required for Op-Amps, RS-232s, audio circuit and sensors to ensure proper biasing and signal range
- * enable symmetrical power supplies
- * Ways to generate:- Charge pump, Inverting Buck boost, Flyback Converters | Virtual Ground (Op-Amps).
- * Dual-Rail Power Supply - (+)ve and (-)ve PSUs

A) Mechanical Switch VS Latch Circuits:-

Cons of Mechanical Switch:- (Vid - 53)

limited lifespan, false trigger in digital circuit, bulkier and less reliable in harsh environment

Latch Circuit Advantage:

Longer lifespan, Clean digital signal, compact suitable with MC.

- * Used as toggle switch, memory storage and control systems

- █ Resettable Fuse :- (Vid - 54)**
- * Multifuse / Polyfuse / Polyswitch
 - * Automatically limit current flow. Once when overcurrent situation occurs, and resets once normal conditions resume.
 - * PPTC Device :- Polymeric Positive Temperature Coefficient
 - * ~~Increase~~ Temp \uparrow Resistance \uparrow Coefficient
 - * Excess current \rightarrow heat up \rightarrow polymer expands \rightarrow disrupts conductive pathway \rightarrow increase in resistance
 - * Automatic reset, cost efficient, compact, versatile

- █ PFC :- (Vid - 55)**
- * PFC - Power Factor Correction
 - * Power Factor =
$$\frac{\text{Real Power}}{\text{Apparent Power}}$$
 - * To address poor power factors.
 - i) Passive PFC :- using inductors and capacitors to counteract the phase diff between I and V
 - ii) Active PFC :- Electronic Circuit, centered around a boost converter topology. Higher PF

□ Color Ring Inductors (Vid-56)

- * Axial Lead Inductors
- * resistor like appearance, colored bands \rightarrow inductance value
- * measured in μH or mH's
- * Application - LC filter, Oscillators,
 - i) LC filter - filter out unwanted signals
 - ii) Oscillator - Generate oscillating signal
 - iii) Boost Converter - store and transfer energy
 - iv) Chokes - block high freq AC signal

□ Ground IS MORE IMPORTANT (Vid-57)

- * Inadequate grounding - signal noise, voltage instability, component failure.

* Proper Grounding should be ensured

Motor Encoders (Vid-5B):-

- * A sensor that provides position and /or speed feedback from the motor shaft.
- * Rotary Encoder - converts angular position to electric signals. Each cycle completes circuit and sends electric signal.

Disadvantages:- no back shaft in every motor, resolution of encoder - 18° per step.

* Magnetic Encoder - 12 bit resolution, 0.033° per step. Cons - good position matters.

* Use in 3d Printers.

* Alternative - stepper motors

* precise speed regulation, accurate position control, better performance in robotics

Surge Protection - (Vid-5g):-

OL \Rightarrow overload

TVS \Rightarrow Transient Voltage Supressor

- * acts as open circuit under normal voltage
- * when a transient voltage exceeds diode's breakdown voltage, acts like Zener diode, passes small current
- * small, easy to add, cheap

- * MOV (Metal Oxide Varistor) :- variable resistance. Works similarly like TVS.
- * Can handle more energy than TVS.
- * GDT (Gas Discharge Tubes) :- Excess energy dissipated as heat. Slower.

■ I²C Protocol (Vid - 60) :-

- * I²C vs I³C :-
- i) Timing - ($I^2C \rightarrow 1\text{MHz}$, $I^3C \rightarrow 12.5\text{MHz}$)
- ii) push-pull drivers, used by I³C
- iii) I³C uses dynamic targeting; reduces addressing data collision.
- iv) Smooth transition from I²C

■ MOSFET Amplifier (Vid - 61) :-

- * BJT can't handle too much current
- * Darlington Transistor - 2 BJT put together, higher current gain and improved drive capability, but increased voltage drop.
- * MOSFET :- amplify signal, tiny voltage drop, less waste of power

⑥

MOSFET \Rightarrow Metal Oxide Semiconductor Field Effect Transistor

⊕ PLC (Vid-62) :-


PLC \Rightarrow Programmable Logic Controller

- * big operating temperature, output - 250V 10A
- * used for industrial input and output
- * bit more expensive than microcontroller
- * function blocks, easy to debug
- * easier wiring, simpler wiring
- * but reaction time is slower than M.C.

Schottky Diode & Zener Diode (Vid - 31) :-

- * Schottky Diode \rightarrow  IN5819
 - * very small conduction loss, low forward voltage drop
 - * Extremely fast switching
 - * High frequency operation
 - * Boost converter - boost a low DC voltage to higher DC voltage - coil, MOSFET, Diode, Capacitor
 - * ~~Low~~ Low blocking voltage \rightarrow cons

- * Zener Diode : 
 - * Zener Voltage

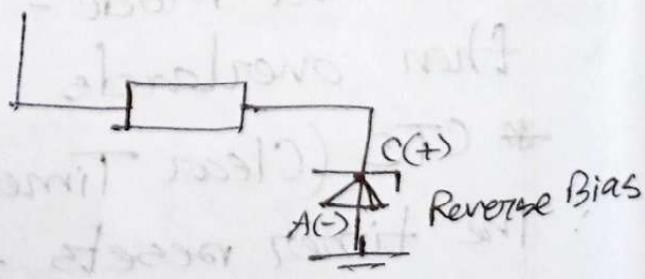

④ Relays and Optocouplers (Vid - 32)

Relay - electromechanical switch

- * sits next to 4 pin ICs

* A coil, two contacts

- * NC - Normally Closed, NO - Normally Open

* contacts open-close via magnetic field

* add flyback diode parallel to coil

- * MOSFET and triac causes power loss

* Galvanically isolated

Optocoupler:

- * Inside \rightarrow led, photosensitive sensor \rightarrow triac / transistor

* Input - output galvanically isolated

* switch faster than relays

* need less activation current

⑤ Strain Gauge / Load Cell and how to use them to measure weight:- (Vid - 33)

* Resistance $120\ \Omega / 370\ \Omega / 1000\ \Omega$

* Resistance changes as the shape changes

* $F \propto E \propto R$ because

* Wheatstone Bridge

* Temperature sensitive but rapid

* Half Bridge

Load Cell :- * aluminium profile

* Wheatstone Bridge is attached

* Connect with HX711 break board - amplifier
ADC circuit

④ Two-position Controller and PID Controller (Vid - 34) :-

* PID - Proportional Integral Derivative

* $F_{mg} = F_a$, gets closer to magnet + turns off
gets far - turns on

* P controller \Rightarrow Output = (Set P - Act v). K_p

* I controller \Rightarrow Diminishes gap with set point

* D controller \Rightarrow Works with the change

⑤ Schmitt Trigger and When to use (Vid - 35)

* comparator resistor \rightarrow Schmitt Trigger

* two threshold values

* avoid noise caused oscillation

* Mechanical switch creates noise oscillation,
Schmitt trigger helps in smooth transition

Q) SPI and How to Use it (Vid-36)

- * SPI \Rightarrow Serial Peripheral Interface
- * 4 main lines:- - MOSI, MISO, SCLK, SS/CS
- * full duplex communication
- * can communicate with multiple slaves
- * high speed communication simple hardware interface no need of device addressing.
- * More pins required, short distance communication and no built-in error checking

Q) What is Impedance (AC Resistance) [Vid-37]

- * Impedance - resistor in AC circuits
- * Two concepts - $\frac{\text{resistance}}{\text{real part}}$ and $\frac{\text{reactance}}{\text{imaginary}}$
- * $Z = R + jX$
- * Inductive Reactance \uparrow frequency \uparrow
- * Capacitive Reactance \downarrow frequency \uparrow
- * Impedance Triangle (Resistance, Reactance, Impedance Magnitude)
- * Capacitors cause current to lead voltage.
Inductors cause current to lag voltage

④ True, Active, Apparent & Deformed Power (Vid-3)

* Energy Multimeter - B probes, can measure electric power and also energy over time in AC appliances


* True Power / Active Power (P) :- This is the actual power consumed by resistive components in a circuit to perform work, (watts)

* Reactive Power (Q) :- Power that oscillates between the source and reactive components (inductors and capacitors), doesn't perform any real work, but essential for maintaining voltage level.

* Apparent Power :- (S) :- $S = \sqrt{P^2 + Q^2}$ (volt-amp)
Represents the total power supplied to the circuit

* Deformed / Distortion Power :- (D) Arises due to non-linear loads that distort the waveform of the current, e.g. electronic devices with rectifiers

* Power Triangle:

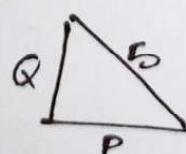

How Shift Registers Work:- (Vid-39)

* controlling large number of ~~leds~~ LEDs using shift register.

* A shift register is a digital memory circuit that takes in data serially (one bit at a time) and outputs in parallel.


* 74HC595 → 8 output pin, serial input clock input, latch input, output enable

* Multiplexing:- only one row is active at a time, shift register outputs define the lit LEDs.

* Program rapidly traverses through all rows


* NPN transistor also used

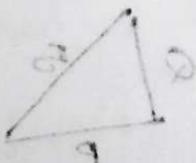* flip-flop:- NOT \rightarrow 1, NAND \rightarrow 4



RFID and NFC :- (Vid-40)


RFID → Radio Frequency Identification

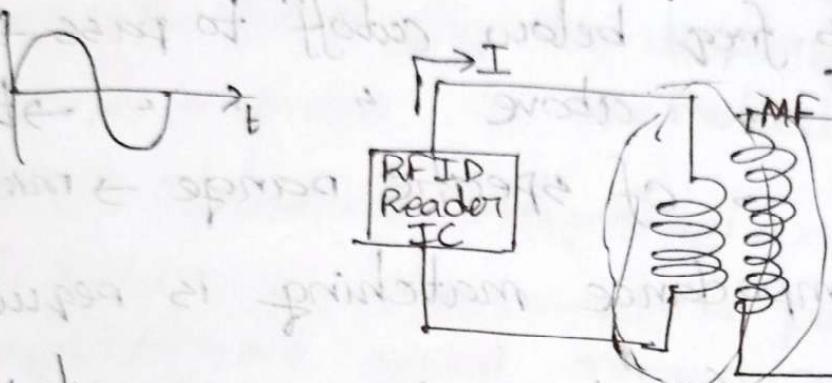

- * the tag also contains a ~~trans~~ coil or antenna and a chip
- * wireless energy transfer

* change in amplitude due to short circuit

NFC → Near Field Communication

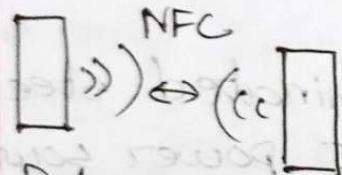

* encrypted via key

* close proximity

Dist. is mandatory

* Transaction limit

DIY Audio Crossover (Vid-41) :- (Passive Filters)

* Audio crossover - electronic circuit that divides an audio signal into separate frequency bands by directing each band to appropriate speaker drivers.

Tweeters - high freq, Midrange Driver - mid freq
Woofers - Low freq

* clearer and more accurate sound production

* Passive crossover utilize resistor, capacitor and inductors to filter audio signal.

LPF :- Allows freq below cutoff to pass \rightarrow woofer

HPF :- \rightarrow above \rightarrow tweeter

BPF :- \rightarrow of specific range \rightarrow midrange driver

* Accurate impedance matching is required


□ Transformers (Vid - 42) :-

* Transformer - steps voltage up or down through electromagnetic induction

* Parts :- core - made from laminated steel plates

Primary Coil - Connected to AC power source

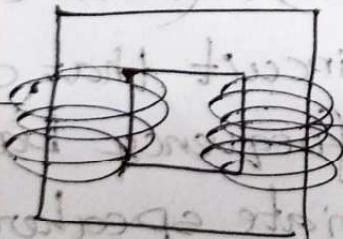Secondary Coil - Delivers transformed voltage to output load



AC flows through h coil - MF in core - changing field induces voltage in the second coil - Faraday's Second Law - Ratio of coil decides

$$\frac{V_s}{V_p} = \frac{n_s}{n_p}$$

Power loss - Copper Wire

Cores - Hysteresis Loss, Eddy Current Loss, Leakage Loss, Dielectric Loss

Controlling Mechanical 7-segment displays:- (Vid - 4B)

- * Mechanical 7-segment display - use physical segments that flip to display digits.
- * each segment is controlled by electromagnet

UART (Universal Asynchronous Receiver/Transmitter)

A hardware communication protocol that enables asynchronous serial communication

RS-485

- An electrical standard that supports serial communication over longer distance

* only defines electronic properties

A

B

Non-inverted and inverted data signal

Improving Electric Longboard with CAN bus:-


* CAN - Controller Area Network (Vid - 4C)

Features:- i) Multi-master capability - allows multiple micro controller communicate without host

ii) Error-detection.

iii) Efficient Communication

* CANH and CANL

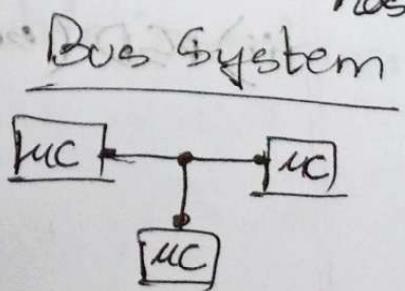

(+) - bus hardware cheap

- * No collision error, ID based system
- * Half-duplex, asynchronous communication

■ Building a Digital Music Player with I²S

(Vid - 45)

* I²S (Inter IC sound) - communication protocol designed for digital audio data transmission between ICs.


* Digital Music Player:-

- i) ESP32 Microcontroller :- main controller
- ii) MAX98357 A.I²S DAC Module :- Converts digital audio data to analog signals
- iii) Speaker - audio output

■ ESP32 - Audio I²S Library

* 3 primary lines:-

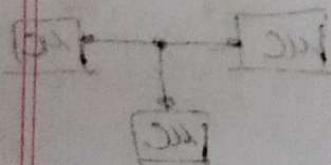
- i) SCK (Serial Clock) :- Sync data transmission
- ii) WS (Word Serial) :- Channel for stereo audio
- iii) RSD (serial data) :- Carries audio data



LNA SWS HNA

④ Asynchronous Motor / Induction Motors - (Vid - 46)

- * most widely used in the world

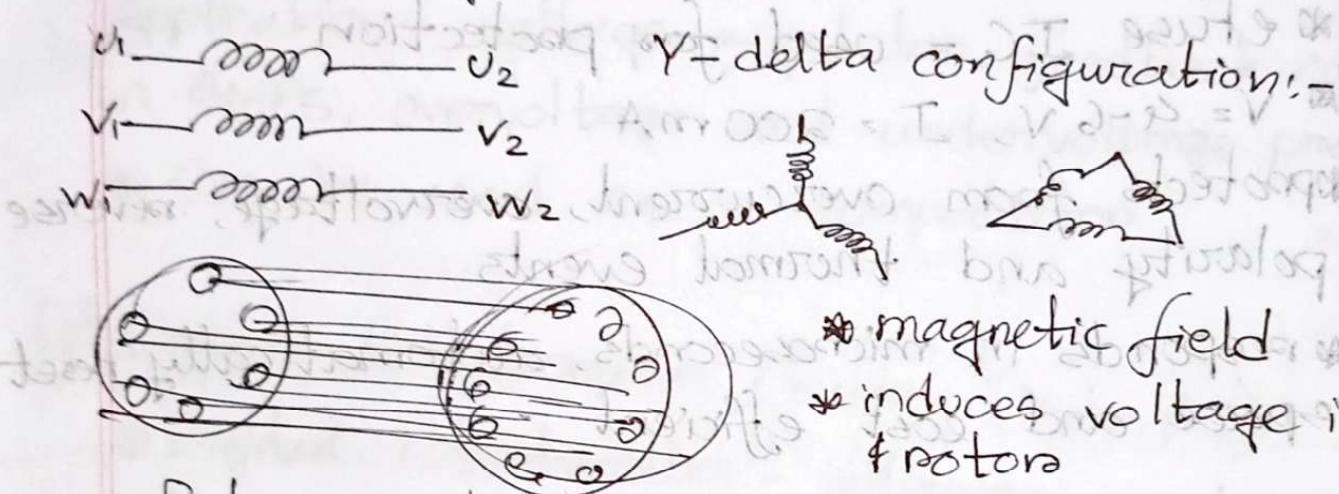

- * magnetic field induces voltage in the rotor

- * Rotor must turn slower than the stator freq.

⑤ Building a Tube Amp? (Vid - 47)

Components:- Vacuum tube (EL34/6VG)

Tube socket, Power Transformer, Output Transformer, Capacitor, Resistor, Potentiometer, Audio Input Jack, Speaker output Terminal, Chassis

* warm and rich sound

* produces more even-order harmonic distortion, which is pleasing to hear

* a softer clipping behaviour while overdriven

④ eFuse + (Vid-48) not M. edon m. bsp. A. (4)

- * Using power bank to power circuit
- * eFuse IC - used for protection
- * $V = 4-6 \text{ V}$, $I = 200 \text{ mA}$
- * protects from overcurrent, overvoltage, reverse polarity and thermal events
- * responds in microseconds, automatically reset
- * space and cost efficient

⑤ Oscilloscope (Vid-49) not team 4098

- * Visualizes voltage and current
- * Amount of channels - 04, bandwidth - 50 MHz
- * low-pass filter, * sampling rate - Higher rate
- * $10 \text{ V} \rightarrow 10 \times \rightarrow 1 \text{ V}$. * scaling factors
- * cursor function - Rise Time

⑥ TL-431 (Vid-50) not m. edon m. bsp. A. (4)

A three terminal adjustable precision shunt regulator

- * Acts like a programmable Zener diode
- * Voltage reference + Error Amplifier + Shunt Regulation

- * Maintains consistent output voltage at changing input voltage / load.
- * Application:- voltage regulator, feedback control in SMPS, overvoltage and undervoltage protection
- * Can be used as a comparator

Digital Potentiometer

- * Digital Potentiometer Guide:- (Vid - 51)
- * Digital Potentiometer - allowing resistance adjustment through digital signals
- * Used for volume control, LCD brightness adjust, turning circuits programmatically
- * I²C or SPI protocol
- * 8 pin IC, Resistor ladder network, MOSFET, Digital Interface
- * Replaces ~~manual~~ manual knob to digital commands

↳ ~~analog~~ digital input output
 12 bits → 4096 steps
 10 bits → 1024 steps
 8 bits → 256 steps
 7 bits → 128 steps
 6 bits → 64 steps
 5 bits → 32 steps
 4 bits → 16 steps
 3 bits → 8 steps
 2 bits → 4 steps
 1 bit → 2 steps

Negative Voltages:- (Vid - 52)

- * Required for Op-Amps, RS-232s, audio circuit and sensors to ensure proper biasing and signal range
- * enable symmetrical power supplies
- * Ways to generate:- Charge pump, Inverting Buck boost, Flyback Converters | Virtual Ground (Op-Amps).
- * Dual-Rail Power Supply - (+)ve and (-)ve PSUs

Mechanical Switch VS Latch Circuits:-

Cons of Mechanical Switch:- (Vid - 53)

limited lifespan, false trigger in digital circuit, bulkier and less reliable in harsh environment

Latch Circuit Advantage:

Longer lifespan, Clean digital signal, compact suitable with MC.

- * Used as toggle switch, memory storage and control systems

- Resettable Fuse :- (Vid - 54)
- * Multifuse / Polyfuse / Polyswitch
 - * Automatically limit current flow. Once when overcurrent situation occurs, and resets once normal conditions resume.
 - * PPTC Device :- Polymeric Positive Temperature Coefficient
 - * ~~Increase~~ Temp ↑ Resistance ↑ Coefficient
 - * Excess current → heat up → polymer expands → disrupts conductive pathway → increase in resistance
 - * Automatic reset, cost efficient, compact, versatile

- PFC :- (Vid - 55)
- * PFC - Power Factor Correction
 - * Power Factor = $\frac{\text{Real Power}}{\text{Apparent Power}}$
 - * To address poor power factors.
 - i) Passive PFC :- using inductors and capacitors to counteract the phase diff between I and V
 - ii) Active PFC :- Electronic Circuit, centered around a boost converter topology. Higher PF

□ Color Ring Inductors (Vid-56)

- * Axial Lead Inductors
- * resistor like appearance, colored bands \rightarrow inductance value
- * measured in μH or mH's
- * Application - LC filter, Oscillators,
 - i) LC filter - filter out unwanted signals
 - ii) Oscillator - Generate oscillating signal
 - iii) Boost Converter - store and transfer energy
 - iv) Chokes - block high freq AC signal

□ Ground IS MORE IMPORTANT (Vid-57)

- * Inadequate grounding - signal noise, voltage instability, component failure.

* Proper Grounding should be ensured

- Motor Encoders (Vid-5B):-
- * A sensor that provides position and /or speed feedback from the motor shaft.
 - * Rotary Encoder - converts angular position to electric signals. Each cycle completes circuit and sends electric signal.
Disadvantages:- no back shaft in every motor, resolution of encoder - 18° per step.
 - * Magnetic Encoder - 12 bit resolution, 0.033° per step. Cons - good position matters.
 - * Use in 3d Printers.
 - * Alternative - stepper motors
precise speed regulation, accurate position control, better performance in robotics

- Surge Protection - (Vid-5g):-
- OL \Rightarrow overload
 - TVS \Rightarrow Transient Voltage Suppressor
 - * acts as open circuit under normal voltage
 - * when a transient voltage exceeds diode's breakdown voltage, acts like Zener diode, passes small current
 - * small, easy to add, cheap

- * MOV (Metal Oxide Varistor) :- variable resistance. Works similarly like TVS.
- * Can handle more energy than TVS.
- * GDT (Gas Discharge Tubes) :- Excess energy dissipated as heat. Slower.

■ I²C Protocol (Vid - 60) :-

- * I²C vs I³C :-
- i) Timing - ($I^2C \rightarrow 1\text{MHz}$, $I^3C \rightarrow 12.5\text{MHz}$)
- ii) push-pull drivers, used by I³C
- iii) I³C uses dynamic targeting; reduces addressing data collision.
- iv) Smooth transition from I²C

■ MOSFET Amplifier (Vid - 61) :-

- * BJT can't handle too much current
- * Darlington Transistor - 2 BJT put together, higher current gain and improved drive capability, but increased voltage drop.
- * MOSFET :- amplify signal, tiny voltage drop, less waste of power

⑥

MOSFET \Rightarrow Metal Oxide Semiconductor Field Effect Transistor

⊕ PLC (Vid-62) :-

PLC \Rightarrow Programmable Logic Controller

- * big operating temperature, output - 250V 10A
- * used for industrial input and output
- * bit more expensive than microcontroller
- * function blocks, easy to debug
- * easier wiring, simpler wiring
- * but reaction time is slower than M.C.