

## Electronic Basics:-

### The Multimeter (vid-01) :-

$$* I = \frac{V}{R} * R = \frac{V}{I} * V = IR$$

\* Multimeter is used to measure voltage, current and resistance.

\* Black Probe  $\rightarrow$  common socket

\* Red Probe  $\rightarrow$  For Voltage & Resistance  $\rightarrow$  V-2Hz

\* Meter Beep  $\rightarrow$  when almost zero resistance, used to check cable break.

\* To check current use high Amp socket

\* Red Probe  $\rightarrow$  (+)ve, Black Probe  $\rightarrow$  (-)ve

### Dimming All kinds of LEDs (vid-02) :-

\* PWM = Pulse Width Modulation

\* Depends upon the voltage

\* Fixed Voltage has to be used, potentiometer causes issue for high power LEDs, waste of energy through Potentiometer.

\* oscilloscope, switching between 5V and 0V

\* Lowering duty cycle  $\rightarrow$  dimming the lights.


\* analogWrite (ledpin, potentiometervalue)

## ④ Programming an ATtiny + Homemade Arduino Shield (Vid-03):-

- \* ATtiny 85 - microcontroller, cost effective, efficient
- \* Building an Arduino Shield
- \* Downloading Arduino Software
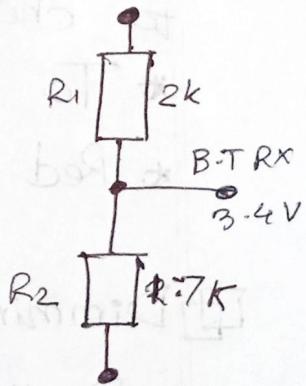
## ④ Arduino + Bluetooth + Android ± Awesome (Vid-04)

- \* Bluetooth Transceiver
- \* Arduino - 5V, B.T Transceiver - 3.3V
- \* TX - Transmit Pin, RX - Receive Pin
- \* S2 Terminal App
- \* Learn Arduino Code



## ④ How to Multiplex (Vid-05)


- \* Controlling Multiple LEDs -
- \* Light up each now individually - multiplex
- \* Arduino UNO
- \* Fewer pins required, efficient control on multiple displays > ideal for clocks, timers and counters.

## ■ Standalone Arduino Circuit :- (Vid - 06)

- \* 16 MHz clock crystal, 22pF capacitor, 10kΩ resistors
- \* Programming ATmega
- \* ICSP = In Circuit Serial Programming.
- \* Making Arduino on Breadboard
- \* No reset switch, no circuit protection, no over-voltage protection.

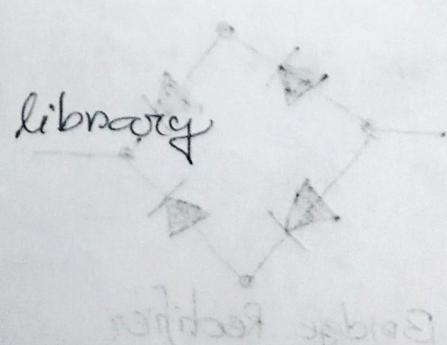
## ■ Segment Display :- (Vid - 07)

- \* 7 Segment Display :- One digit in one case, or two digits in one case.
- \* Check datasheet - 2.1 Volts
- \* Using PCB for displaying number
- \* 4 pin binary counter
- \* Adding push button / sensor to count number
- \* Using multiplexing , on a number IC
- \* Controls 4 digits, multiplexing 2 digits at a time
- \* Using cool-SAA1064 library




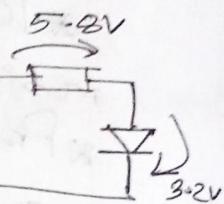
## ④ Everything about LEDs and Current Limiting Resistors (Vid - 8)

- \* Forward Voltage and Current
- \* Careful about power, burn resistor
- \* Small voltage change in power source can destroy all LEDs. Solution - using small resistors.
- \* Use LED in constant current, not constant voltage
- \* Use constant current driver






## ⑤ Diodes and Bridge Rectifiers :- (Vid-09)

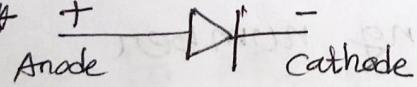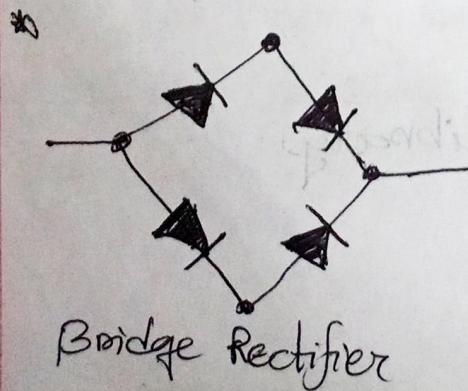- \* Diode prevents current flow to other way.
- \*  Voltage drop exists, waste of power
- \* AC  $\rightarrow$  DC
- \* Calculated in RMS Value




Bridge Rectifier
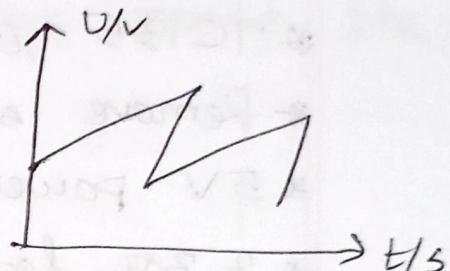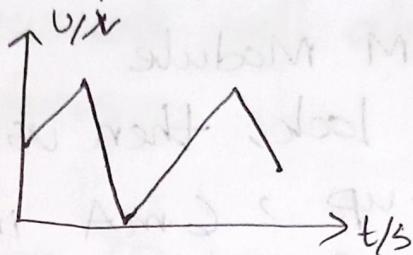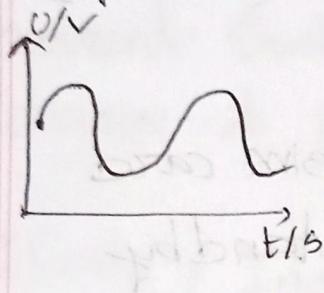
## Digital to Analog Converter (DAC) (Vid-10)



\* 8 bit R-R DAC

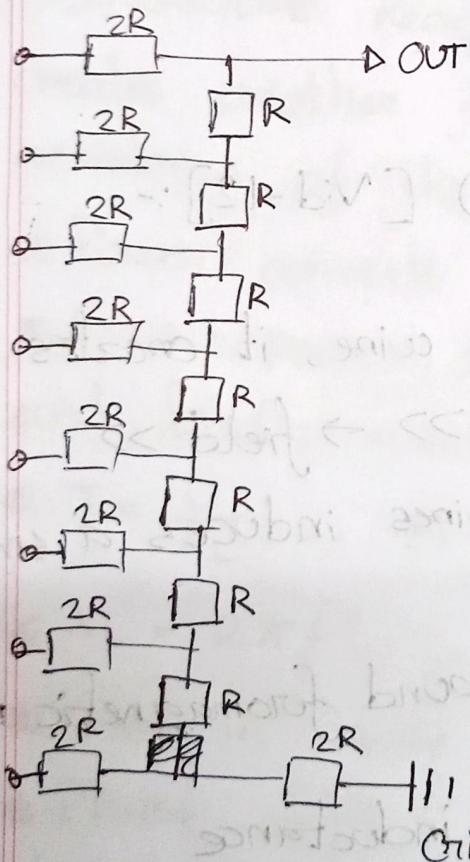


\* Ramp function, triangle function

\* Connect speaker via voltage follow-up

\* DAC-0800

\* Analog-write function

\* LC Low pass filter:-

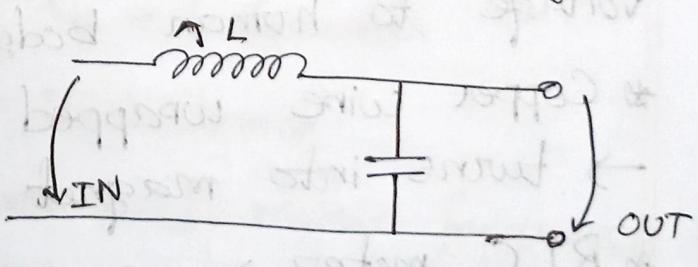

\* 12 bit DAC - audio filter, DAC generators

## Sending SMS Using Arduino (Vid-11)

- \* TC 35 • GSM Module
- \* Remove sim lock, then use sim card
- \* 5V power-up, 6mA in standby
- \* 3.3V logic level, 9600 baud rate
- \* Use as alarm system

## Coils / Inductors (Part-01) [Vid-12]:-

- \* Basics of inductors
- \* When current flows through wire, it creates magnetic field around it.  $\text{current} \gg \rightarrow \text{field} \gg$
- \* The magnetic field of wires induces a small voltage to human body
- \* Copper wire wrapped around ferromagnetic metal  $\rightarrow$  turns. into magnet
- \* RLC meter  $\rightarrow$  measures inductance
- \* Lenz Law:-  $W = \frac{1}{2} J^2$
- \* flyback diode to protect switch
- \* The voltage at circuits lets current flow. This current starts creating a magnetic field, which

induces voltage to the coil itself, produces induced current. Such current will always oppose the change it produces.

## Coils / Inductors (Part - 02) [Vid-13]:-

\* **Inductive Reactance**:- The inductance of an inductor creates another form of resistance aside the resistance of the wire, this is called reactance.

\* Power converts into magnetic field

\* **Cons**:- Power oscillates between voltage source and load; reactive power

$$\text{# } I = \frac{U}{X_L}, \uparrow F \rightarrow \uparrow X_L \rightarrow \downarrow \text{Current}$$

$$\text{# } X_L = 2\pi f L, L = \text{Inductance}$$

\* Use in noise filter and music frequency filter

\* Phase shift  $\rightarrow$  inductance in circuit

\* Alternate to RLC meter  $\rightarrow$  transistor tester

## 4) Capacitors:- (Vid-14)



\* Dielectric material like water increases capacitance.

\* Electrolytic Capacitor  $\rightarrow$  metal sheet with dielectric material within it.

\* Reversing polarity destroys

\* Basic capacitor  $\rightarrow$  metal sheet with dielectric substance in the middle

\* Increasing capacitance - bringing the plates closer, using dielectric.

\* Switching operation  $\rightarrow$  creates different signals using resistors, creates capacitive reactance ( $X_C$ )

\* Capacitance  $\downarrow$  current  $\downarrow$


\* Frequency  $\downarrow$  current  $\downarrow$

$$X_C = \frac{1}{2\pi f C}$$

\* creates phase shift,
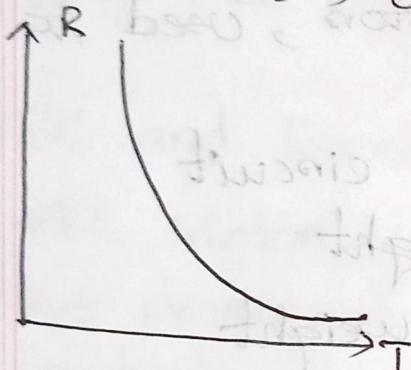
## ④ Temperature Measurement (Part - 01) [Vid - 15]

- \* NTC = Negative Temperature Coefficient, thermister
- \* Resistors → decrease value as temperature rises




\* PT - 100,  $0^\circ\text{C} \rightarrow 100\Omega$   
Resistance increases with higher Temperature  $\rightarrow \text{max} \rightarrow 250^\circ\text{C}$

\* Voltage offset

- \* Wheatstone Bridge  $\rightarrow$  temperature calculating via the change of resistance
- \* 10 - turn potentiometer / pre-made transmitter
- \* Voltage drop  $\rightarrow$  analog input
- \* LCD connect  $\rightarrow$  shows temperature
- \* LM 35  $\rightarrow$  IC ( $0-1.5\text{ V}$ ,  $0-150^\circ\text{C}$ )
- \* Thermal Inertia
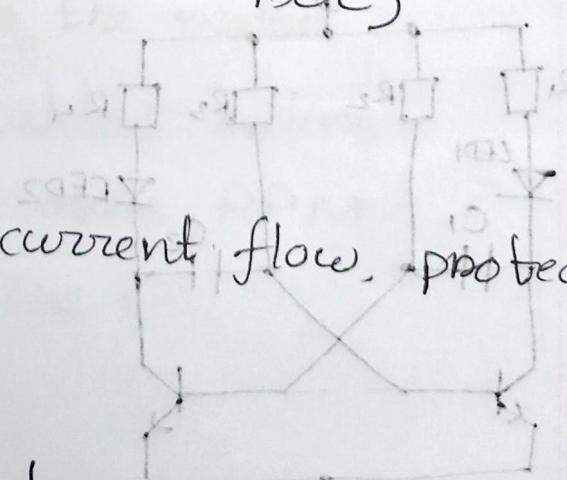
## ④ Resistors [Vid - 16] :-


- \* Resists the excess current flow, protecting equipment
- \* Power Resistors
- \* Series  $\rightarrow$  voltage divider
- \* 5V data signal to 3.3V signal



- \* Pull-down resistor - pulls to ground level
- \* Pull-up resistor
- \* Shunts,  $\rightarrow$  small value resistors, used to build load
- \* Used as fuses to protect circuit
- \* Photoresistor  $\rightarrow$  detect light
- \* Strain Gauge  $\rightarrow$  measure weight
- \* AC 50 Hz Sine voltage  $\rightarrow$  don't produce phase shift
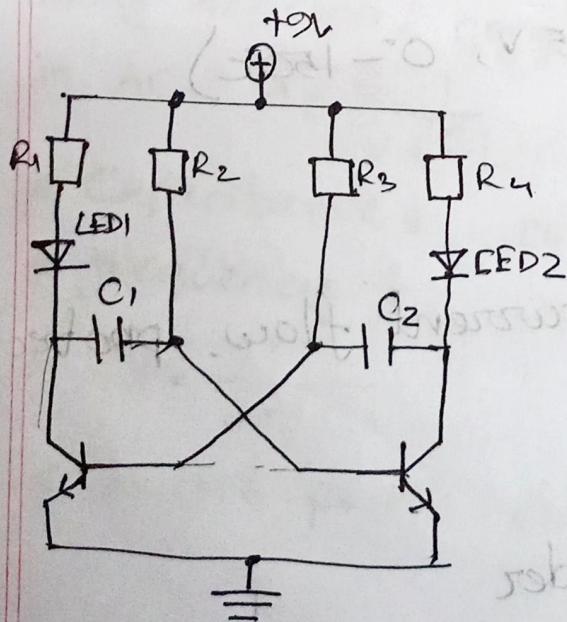
## □ Oscillator [Vid-17] :-

- \* Oscillator - creates periodic alternate voltage signals
- \* Relaxation Circuit (R-C) :-



- \* Create rectangle wave
- \* LC Resonator, tank circuits
- \* Parasitic Resistance
- \*  $|X_C| = |X_L|$
- \* Resonance frequency
- \* Using amplifier - stable MHz sine wave

\* Crystal oscillator  $\rightarrow$  more stable frequency  
works like L.C resonators, mechanical vibration  
of a PZT crystal.

## ② DC and Brushless DC Motor + ESC (Vid - 12)

\* DC Motor:- uses direct current for rotary movement  
two permanent magnets of opposite polarity  
(stator), rotor consists of 5 coils connected to  
the commutator, two copper brushes


\* Brushless motor - electrical circuit  
to create magnetic field.

\* ESC  $\rightarrow$  Electric Speed Controller

\* Total current consumption depends on what  
load is connected to the motor

\* High torque  $\rightarrow$  brushless motors

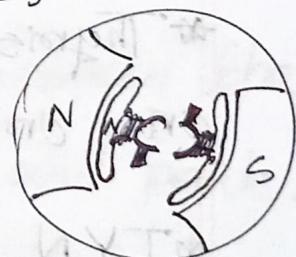\* More KV rating  $\rightarrow$  more RPM




## Q) I<sup>2</sup>C and How to Use it [Vid-19]

- \* I<sup>2</sup>C → Two-wire interface, popular comm. protocol that allows one or more master devices to talk to upto 112 slave devices
- \* Point out data sheet
- \* wire library
- \* address-fixed 7 bit value
- \* PLL value
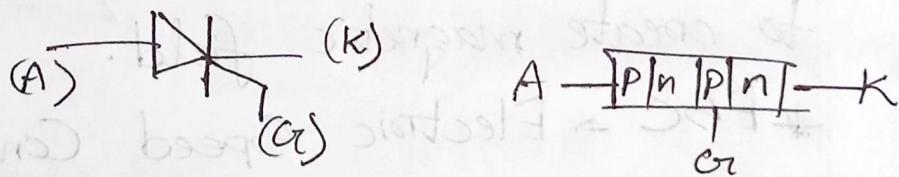
## Q) Thyristor, Triac II. Phase Angle Control [Vid-20]

- \* Thyristor - controllable diode, can't be turned on or off
- \* TYN 604
- \* Latching Current
- \* MOSFET → used as switch
- \* turnoff time
- \* Triac
- \* fe-radical schematic
- \* Cons:- constantly decreasing power factor




## Q) OpAmp (Operational Amplifier) [Vid - 21] :-

- \* 8 pins / 14 pins
- \* The output of an OpAmp will always attempt everything to keep Voltage diff. between inputs at 0 V.
- \* Amplify signal from a sensor
- \* DC Offsets
- \* Rail - to - Rail Op Amp  $\rightarrow$   $V_{\text{output}} = V_{\text{supply}}$
- \* Input Draws no current
- \* When no feedback is attached between the outputs and inputs; the outputs will peak.
- \* Comparator IC
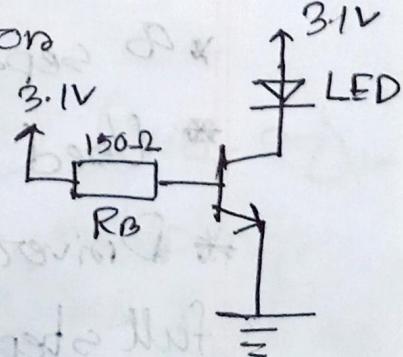
## B) Transistor as a switch (BJT) [Vid - 22]

- \* BJT = Bipolar Junction Transistor
- \* Use as switch, on: amplifier
- \* Base, Emitter, Collector
- \* Heating Issue as switch




## □ Transistor (MOSFET) as a switch - [Vid-2]

- \* MOSFET  $\rightarrow$  0.6 W energy loss, 97% efficiency
- \* Two types - N channel and P channel
- \*  $G > \text{Voltage} > T.V$
- \* Electrostatic voltage of body can turn on the loads, put resistor to prevent so
- \* Bootstrapping - P channel MOSFET, pull-up
- \* ~~1.15~~ 1.15  $\Omega$  resistor between gate and Anode
- \* Gate, Source, Drain
- \* Energy loss at the gate


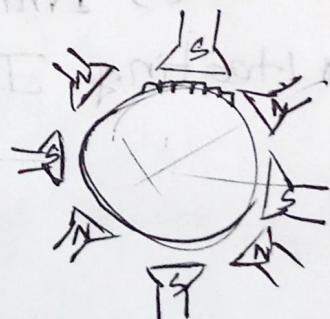
## □ Stepper Motors and How to Use them [Vid-24]

- \* Stepper Motors - Hybrid Synchronous, 4 magnets, 50 teeth per sprocket
- \* 8 separate coil motors
- \* Used in 3D printers
- \* Drivers - wave driving, full step / half step driving



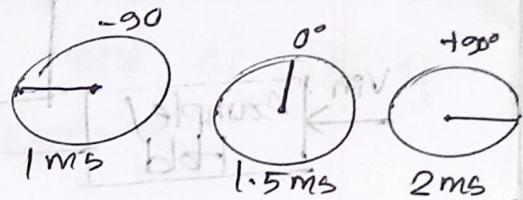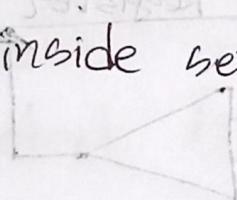
## ④ Servos and How to Use them (Vid-25):-

- \* Servo :- Motor driven positioning system
- \* Ground, VCC, Control Signal
- \* Potentiometer inside servo
- \* H-Bridge
- \* N channel, P channel mosfets
- \* Servo library
- \* Gear DC motor for 360° rotation



## ④ 555 timer IC (Vid-26):-

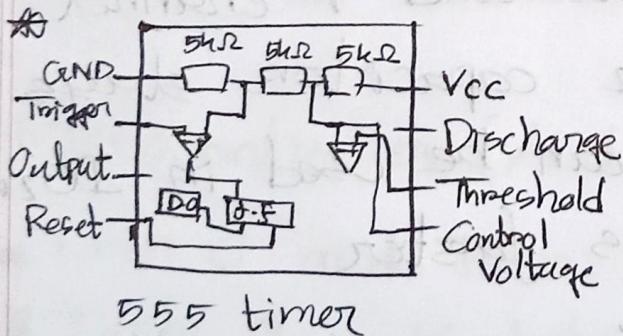


\* monostable multivibrator configuration

\* Two additional diodes

## ④ ADC (Analog to Digital Converter) (Vid-27):-

- \* Nyquist - Shannon Theorem :- The sampling Rate should be at least twice as high as the frequency of the signal.

## \* Sampling rate

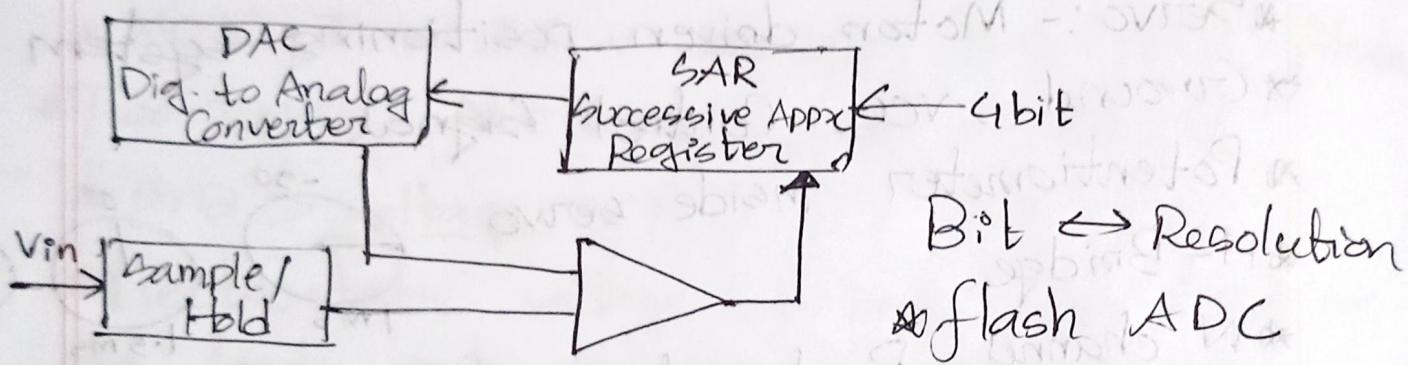

## ■ IGBT and When to Use them (Vid - 28):-

- \* IGBT = Insulated Gate Bipolar Transistor
- \* 2 types - N channel and P channel.
- \* Gate behaves like capacitor, stays on
- \* MOSFET Driver can be used in IGBT
- \* MOSFET switches faster
- \* IGBT  $< 200$  kHz
- \* IGBT has greater power loss (32 times)

## ④ Solar Panel and Charge Controller (Vid- 29)

- \* Individual Solar Cells, when exposed to light, creates electrical energy
- \* Charge Controllers:- manage the charging process and protect the batteries.
- \* 2 types:- PWM:- simpler cost efficient option that reduces the voltage of solar panel to match the battery voltage
- MPPT:- A more advanced and efficient controller targets at harvesting maximum power

## ⑤ Microcontroller (Arduino) Timers (Vid- 30)

- \* Timer 0 and Timer 2 :- 8 bit timer
- \* Timer 1 :- 16 bit timer
- \* Normal Mode:- counts upto maximum value, then overloads
- \* CTC (Clear Timer on Compare Match) Mode:- The timer resets matching specified mode
- \* PWM:- Used to control motors and LEDs

\* Configuring Timers:-

TCCRnA and TCCRnB

OCRnA / OCRnB

TIMSKn